

# Verification of KCL for AC Circuits

## EXP 8 Report

**Course No: EEE 164**

Experiment No: 08  
Department: CSE  
Sec: B2

**Student ID: 2405103**  
Name: Kazi Md. Raiyan  
Lab Group No: 03

Date of Performance: 12.07.2025  
Date of Submission:

**Partners' Student ID:**  
2405104  
2405105  
2405106  
2405107  
2405108

# 1 Objectives

This experiment is designed to:

- Verify KCL for AC circuits.

Upon successful completion of this experiment, we should be able to:

- Construct RLC circuits.
- Understand the validity of analytical methods used in theory.

# 2 Apparatus

1. Function Generator
2. Oscilloscope
3. Multimeter
4. Two  $100\ \Omega$  resistors
5. One  $120\ \Omega$  resistor
6. One  $1\ \mu\text{F}$  capacitor
7. Breadboard

The ratings of the equipment supplied were checked.

### 3 Experimental Setup

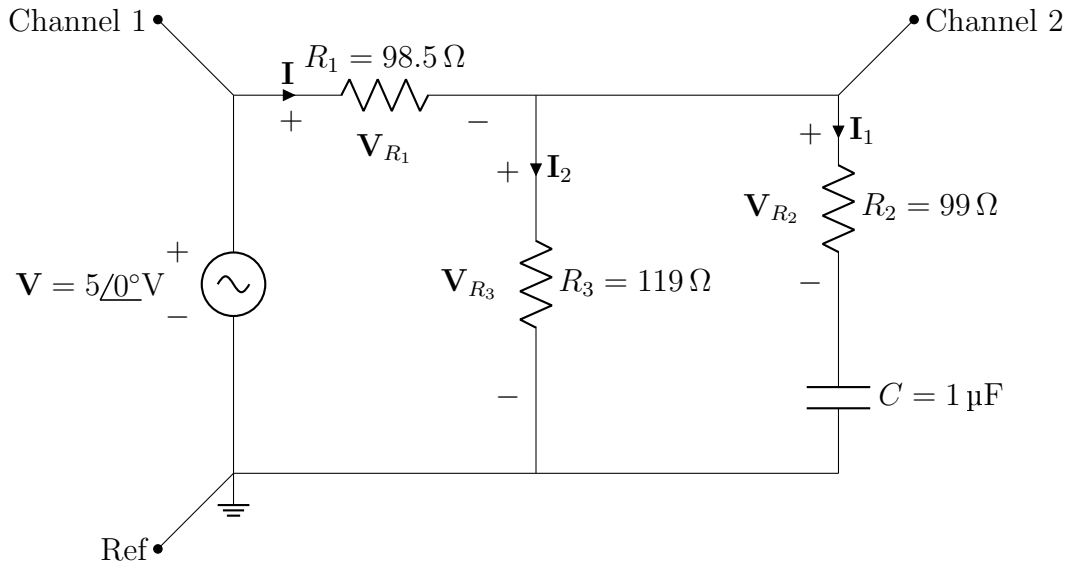


Fig 1: Circuit 1

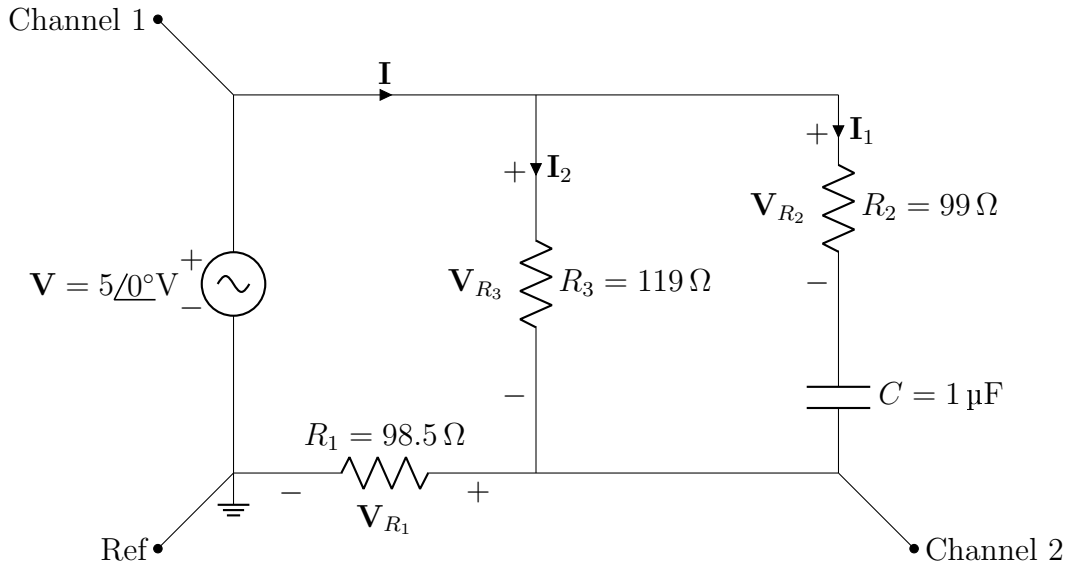


Fig 2: Circuit 2

### 4 Procedure

1. The resistance of the resistors was measured with the help of the multi-meter and the values were written down the table below.

2. The frequency,  $f$  of the function generator was set at 1 kHz. The power source was not turned on yet.
3. At first, circuit was setup as shown in Fig 1.
4. Then the magnitude and phase of the voltage  $\mathbf{V}_{R_3}$  were determined using the multimeter and the oscilloscope respectively.
5. Then the phasor currents  $\mathbf{I}_1 = \mathbf{I}_{R_2} = \mathbf{I}_C = \frac{\mathbf{V}_{R_3}}{Z_{RC}}$  and  $\mathbf{I}_2 = \frac{\mathbf{V}_{R_3}}{R_3}$  were determined mathematically, where  $Z_{RC}$  is the equivalent impedance of  $R_2$  and  $C$ .
6. Then the circuit was setup as shown in Fig 2.
7. Then the magnitude and phase of the voltage  $\mathbf{V}_{R_1}$  were determined using the multimeter and the oscilloscope respectively.
8. Then the phasor current  $\mathbf{I} = \mathbf{I}_{R_1} = \frac{\mathbf{V}_{R_1}}{R_1}$  was determined mathematically.
9. Then the phasor voltage  $\mathbf{V}_{R_2}$  was determined mathematically.
10. The steps 3-9 were repeated for 500 hertz and 2 kHz source frequency.
11. The phasor values of  $\mathbf{I}$ ,  $\mathbf{I}_1$  and  $\mathbf{I}_2$  were determined theoretically for the three frequencies and compared to the experimentally found values.

## 5 Data Collection

### Measurements:

$$R_1 = 98.5 \Omega$$

$$R_2 = 99 \Omega$$

$$R_3 = 119 \Omega$$

**Table:**

$f(\text{kHz})$	$\mathbf{V}_{R_2}(\text{V})$	$\mathbf{V}_{R_3}(\text{V})$	$\mathbf{I}_1(\text{mA})$	$\mathbf{I}_2(\text{mA})$	$\mathbf{V}_{R_1}(\text{V})$	$\mathbf{I}(\text{mA})$	$\mathbf{I}_1 + \mathbf{I}_2(\text{mA})$
0.5	0.55/66.6°	2.01/-6.12°	6.03/66.6°	16.89/-6.12°	1.89/6.48°	19.19/6.48°	19.55/11.01°
1	0.82/50.9°	1.72/-7.2°	9.17/50.9°	14.45/-7.2°	2.02/7.2°	20.5/7.2°	20.8/14.77°
2	1.02/30.15°	1.45/-8.64°	11.4/30.15°	12.18/-8.66°	2.09/7.2°	21.22/7.2°	22.24/10.07°

Table 1: Experimental values

## 6 Report

### 6.1 Theoretically calculate all the values written in the table.

For  $f = 0.5 \text{ kHz}$ :

$$\omega = 2\pi f = 3.141 \times 10^3 \text{ rad} \cdot \text{s}^{-1}$$

$$Z_C = -\frac{1}{\omega C}j = -318.310j\Omega$$

$$\therefore Z_{eq} = R_1 + (R_3^{-1} + (R_2 + Z_C)^{-1})^{-1} = 199.076/\underline{-8.75^\circ}\Omega$$

$$\therefore \mathbf{I} = \frac{V}{Z_{eq}} = 25.116/\underline{8.75^\circ}\text{mA}$$

Now using the current divider rule:

$$\mathbf{I}_1 = \frac{R_3}{R_3 + R_2 + Z_{RC}}\mathbf{I} = 7.747/\underline{64.34^\circ}\text{mA}, \text{ and}$$

$$\mathbf{I}_2 = \frac{R_2 + Z_{RC}}{R_3 + R_2 + Z_{RC}}\mathbf{I} = 21.701/\underline{-8.38^\circ}\text{mA}$$

$$\therefore \mathbf{V}_{R_1} = \mathbf{I}R_1 = 2.474/\underline{8.75^\circ}\text{V}$$

$$\therefore \mathbf{V}_{R_2} = \mathbf{I}_1 R_2 = 0.767/\underline{64.34^\circ}\text{V}$$

$$\therefore \mathbf{V}_{R_3} = \mathbf{I}_2 R_3 = 2.582/\underline{-8.38^\circ}\text{V}$$

For  $f = 1 \text{ kHz}$ :

$$\omega = 2\pi f = 6.283 \times 10^3 \text{ rad} \cdot \text{s}^{-1}$$

$$Z_C = -\frac{1}{\omega C}j = -159.155j\Omega$$

$$\therefore Z_{eq} = R_1 + (R_3^{-1} + (R_2 + Z_C)^{-1})^{-1} = 177.835/\underline{-10.02^\circ}\Omega$$

$$\therefore \mathbf{I} = \frac{V}{Z_{eq}} = 28.116/\underline{10.02^\circ}\text{mA}$$

Now using the current divider rule:

$$\mathbf{I}_1 = \frac{R_3}{R_3 + R_2 + Z_{RC}}\mathbf{I} = 12.396/\underline{46.15^\circ}\text{mA}, \text{ and}$$

$$\mathbf{I}_2 = \frac{R_2 + Z_{RC}}{R_3 + R_2 + Z_{RC}}\mathbf{I} = 19.524/\underline{-11.97^\circ}\text{mA}$$

$$\therefore \mathbf{V}_{R_1} = \mathbf{I}R_1 = 2.769/\underline{10.02^\circ}\text{V}$$

$$\therefore \mathbf{V}_{R_2} = \mathbf{I}_1 R_2 = 1.227/\underline{46.15^\circ}\text{V}$$

$$\therefore \mathbf{V}_{R_3} = \mathbf{I}_2 R_3 = 2.323/\underline{-11.97^\circ}\text{V}$$

For  $f = 2 \text{ kHz}$ :

$$\omega = 2\pi f = 1.257 \times 10^4 \text{ rad} \cdot \text{s}^{-1}$$

$$Z_C = -\frac{1}{\omega C}j = -79.577j\Omega$$

$$\therefore Z_{eq} = R_1 + (R_3^{-1} + (R_2 + Z_C)^{-1})^{-1} = 161.54/\underline{-7.44^\circ}\Omega$$

$$\therefore \mathbf{I} = \frac{V}{Z_{eq}} = 30.95/\underline{7.44^\circ}\text{mA}$$

Now using the current divider rule:

$$\mathbf{I}_1 = \frac{R_3}{R_3 + R_2 + Z_{RC}} \mathbf{I} = 15.871/\underline{27.50^\circ}\text{mA, and}$$

$$\mathbf{I}_2 = \frac{R_2 + Z_{RC}}{R_3 + R_2 + Z_{RC}} \mathbf{I} = 16.941/\underline{-11.30^\circ}\text{mA}$$

$$\therefore \mathbf{V}_{R_1} = \mathbf{I}R_1 = 3.049/\underline{7.44^\circ}\text{V}$$

$$\therefore \mathbf{V}_{R_2} = \mathbf{I}_1 R_2 = 1.571/\underline{27.50^\circ}\text{V}$$

$$\therefore \mathbf{V}_{R_3} = \mathbf{I}_2 R_3 = 2.016/\underline{-11.30^\circ}\text{V}$$

**Table:**

$f(\text{kHz})$	$\mathbf{I}(\text{mA})$	$\mathbf{I}_1(\text{mA})$	$\mathbf{I}_2(\text{mA})$	$\mathbf{V}_{R_1}(\text{V})$	$\mathbf{V}_{R_2}(\text{V})$	$\mathbf{V}_{R_3}(\text{V})$
0.5	25.116/ <u>8.75°</u>	7.747/ <u>64.34°</u>	21.701/ <u>-8.38°</u>	2.474/ <u>8.75°</u>	0.767/ <u>64.34°</u>	2.582/ <u>-8.38°</u>
1	28.116/ <u>10.02°</u>	12.396/ <u>46.15°</u>	19.524/ <u>-11.97°</u>	2.769/ <u>10.02°</u>	1.227/ <u>46.15°</u>	2.323/ <u>-11.97°</u>
2	30.95/ <u>7.44°</u>	15.871/ <u>27.50°</u>	16.941/ <u>-11.30°</u>	3.049/ <u>7.44°</u>	1.571/ <u>27.50°</u>	2.016/ <u>-11.30°</u>

Table 2: Theoretical values

**6.2** Draw the phasor diagrams for both the circuits of Fig 1 and Fig 2 for  $f = 1$  kHz source frequency using the theoretical values. The diagrams should be drawn to scale on graph paper.

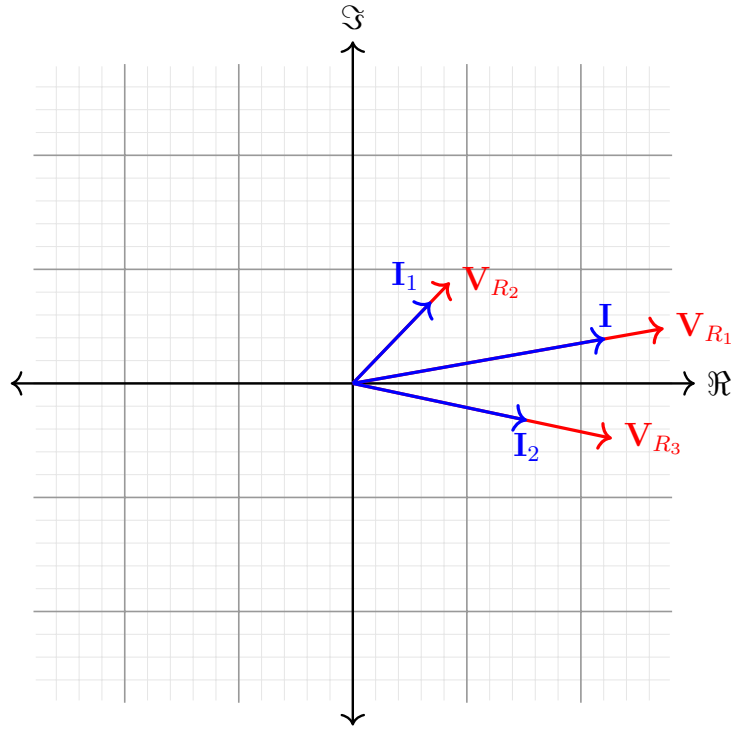


Fig 3: Phasor Diagram for Circuit 1 and Circuit 2 at  $f = 1$  kHz

The phasor diagram for Circuit 1 and Circuit 2 is the same, because the circuits are essentially the same.

**6.3** From the phasor diagram, express the voltages and the currents as phasors and compare those with the values in table 1 for  $f = 1$  kHz.

From the phasor diagram, the voltages and currents at  $f = 1$  kHz are:

- $\mathbf{V}_{R_1} = 2.769/\underline{10.02^\circ}$  V
- $\mathbf{V}_{R_2} = 1.227/\underline{46.15^\circ}$  V
- $\mathbf{V}_{R_3} = 2.323/\underline{-11.97^\circ}$  V
- $\mathbf{I} = 28.116/\underline{10.02^\circ}$  mA
- $\mathbf{I}_1 = 12.396/\underline{46.15^\circ}$  mA

- $\mathbf{I}_2 = 19.524/-11.97^\circ$  mA

Comparing these theoretical phasor values with the experimental values in Table 1 for  $f = 1$  kHz:

	$\mathbf{V}_{R_1}$ (V)	$\mathbf{V}_{R_2}$ (V)	$\mathbf{V}_{R_3}$ (V)	$\mathbf{I}$ (mA)	$\mathbf{I}_1$ (mA)	$\mathbf{I}_2$ (mA)
Theoretical	2.769/10.02°	1.227/46.15°	2.323/-11.97°	28.116/10.02°	12.396/46.15°	19.524/-11.97°
Experimental	2.02/7.2°	0.82/50.9°	1.72/-7.2°	20.5/7.2°	9.17/50.9°	14.45/-7.2°

Table 3: Comparison of Theoretical and Experimental Values at  $f = 1$  kHz

The experimental values are close to the theoretical values, with some differences due to measurement errors, non-ideal components, and faulty apparatus. Regardless, they confirm the validity of the theoretical analysis.

#### 6.4 Show that the currents noted in table 1 satisfy KCL for all three frequencies.

We can verify KCL by checking if the sum of the currents entering a node equals the sum of the currents leaving that node. Which means we need to check if  $\mathbf{I} = \mathbf{I}_1 + \mathbf{I}_2$  holds true.

For  $f = 0.5$  kHz:

From Table 1, we have:  $\mathbf{I} = 19.19/6.48^\circ$  mA

$\mathbf{I}_1 + \mathbf{I}_2 = 19.55/11.01^\circ$  mA

$\therefore \mathbf{I} \approx \mathbf{I}_1 + \mathbf{I}_2$

For  $f = 1$  kHz:

From Table 1, we have:  $\mathbf{I} = 20.5/7.2^\circ$  mA

$\mathbf{I}_1 + \mathbf{I}_2 = 20.8/14.77^\circ$  mA

$\therefore \mathbf{I} \approx \mathbf{I}_1 + \mathbf{I}_2$

For  $f = 2$  kHz:

From Table 1, we have:  $\mathbf{I} = 21.22/7.2^\circ$  mA

$\mathbf{I}_1 + \mathbf{I}_2 = 22.24/10.07^\circ$  mA

$\therefore \mathbf{I} \approx \mathbf{I}_1 + \mathbf{I}_2$

It can be seen that the currents satisfy KCL for all three frequencies, as the sum of the currents entering the node is approximately equal to the sum of the currents leaving the node.

#### 6.5 Explain why we couldn't measure all the voltages with the circuit shown in fig 1. Why it was essential to setup the circuit shown in fig 2?